

EE530L: Homework 1

- ① Find the equivalent resistances between each of the terminal pairs (1,2), (2,3), and (3,1) in figure 1.

Use Y-Δ

transformation:

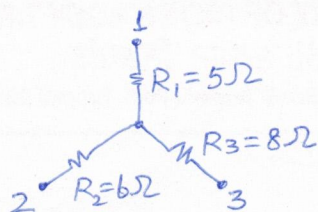


Figure 1

$$R_{12} = R_1 + R_2 + \frac{R_1 R_2}{R_3} = \boxed{14.75\Omega}$$

$$R_{23} = R_2 + R_3 + \frac{R_2 R_3}{R_1} = \boxed{22\Omega}$$

$$R_{31} = R_3 + R_1 + \frac{R_3 R_1}{R_2} = \boxed{19.67\Omega}$$

- ② Solve for the current i flowing through impedance Z_0 in Fig. 2. Assume $v, i_1, i_2, Z_1, \dots, Z_7$ are all given.

Use KVL around
ADB.

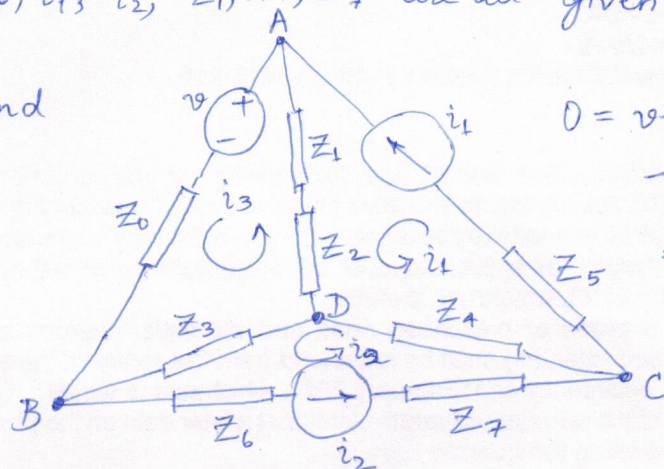


Figure 2

$$0 = v + i_3(Z_0 + Z_3 + Z_1 + Z_2) - i_1(Z_1 + Z_2) - i_2 Z_4$$

$$\Rightarrow i = i_3 = \boxed{\frac{i_1(Z_1 + Z_2) + i_2 Z_4 - v}{Z_0 + Z_1 + Z_2 + Z_3}}$$

- ③ How many linearly independent currents exist in the network/circuit shown in Figure 3? Assume all the blobs are passive two terminal networks.

Use Euler's
formula.

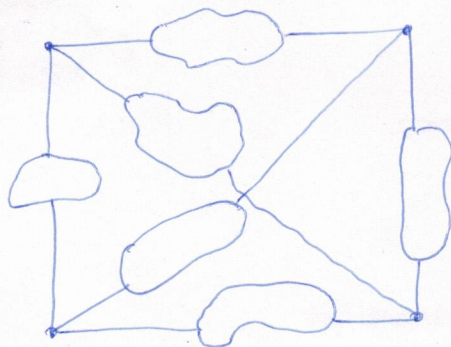




Figure 3

$$V - E + F = 1$$

$$F = 1 + E - V$$

$$= 1 + 6 - 4 = \boxed{3}$$

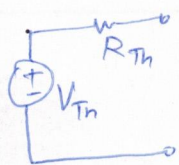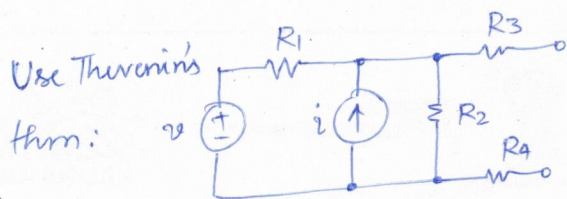- ④ If the two circuits in Fig. 4 are equivalent as seen from the 2 terminals, find v_{Th} and R_{Th} .





$$V_{Th} = \frac{\frac{v}{R_1} + i}{\frac{1}{R_1} + \frac{1}{R_2}}$$

$$R_{Th} = \frac{R_1 R_2 + R_3 + R_4}{R_1 + R_2}$$

Figure 4

- ⑤ If the two circuits in Fig. 5 are equivalent as seen from the two terminals, find i_{No} and R_{No} .

Use Norton's thm:

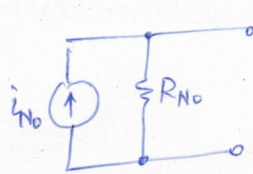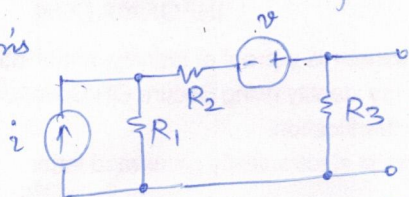


$$i_{No} = \frac{v + i R_1}{R_1 + R_2}$$

$$R_{No} = \frac{R_3 (R_1 + R_2)}{R_1 + R_2 + R_3}$$

Figure 5

- ⑥ Solve for the voltage across Z_0 in the circuit of Fig. 6.

Apply ~~KVL~~ KCL at node 1:

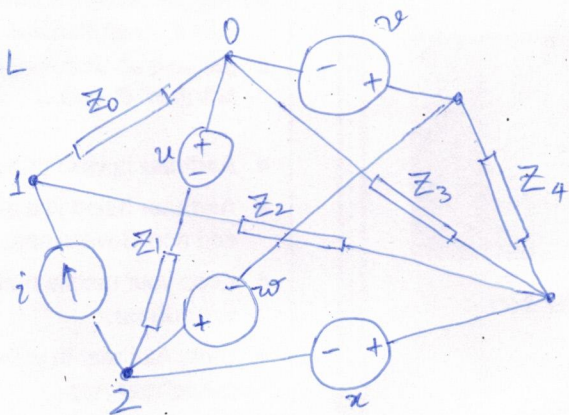

w.l.o.g. $v_0 = 0$.


$$\frac{v_1}{Z_0} + \frac{v_1 - (v + w + x)}{Z_2} = i$$

$$\Rightarrow v_1 = \frac{\frac{v + w + x}{Z_2} + i}{\frac{1}{Z_0} + \frac{1}{Z_2}}$$

Figure 6

- ⑦ Find voltage at node 0 in the circuit of Fig. 7. Assume $v_1, v_2, v_3, v_4, i_5, R_1, R_2, L_3, C_4, R_6$ are all known.

Use Millman's thm:

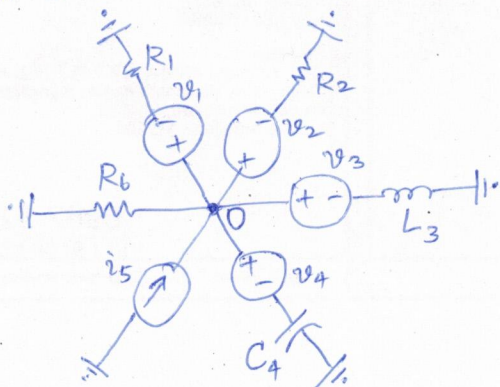

$$v_0 = \frac{\frac{v_1}{R_1} + \frac{v_2}{R_2} + \frac{v_3}{sL_3} + v_4 sC_4 + i_5}{\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{sL_3} + sC_4 + \frac{1}{R_6}}$$

Figure 7

⑧ Find (i) R_L given R_S , and (ii) R_S given R_L , for

(a) maximum power transfer from source v_s to load R_L ;

(b) maximum efficiency.

Use max. power
transfer &
efficiency thms:

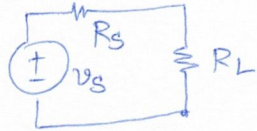


Figure 8

(ai) $R_L = \boxed{R_S}$.

(aii) $R_S = \boxed{0}$.

(bi) $R_L = \boxed{\infty}$.

(bii) $R_S = \boxed{0}$.