

EE530L: Home work 1

- ① Find the equivalent resistances between each of the terminal pairs (1,2), (2,3), and (3,1) in figure 1.

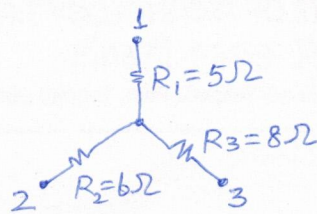


Figure 1

- ② Solve for the current i flowing through impedance Z_0 in Fig. 2. Assume v , i_1 , i_2 , Z_1, \dots, Z_7 are all given.

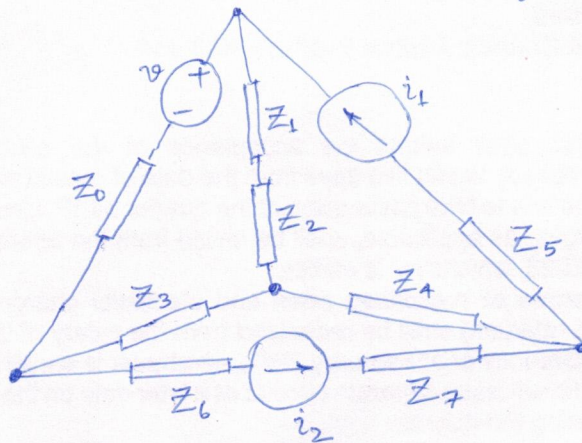


Figure 2

- ③ How many linearly independent currents exist in the network/circuit shown in Figure 3? Assume all the blobs are passive two terminal networks.

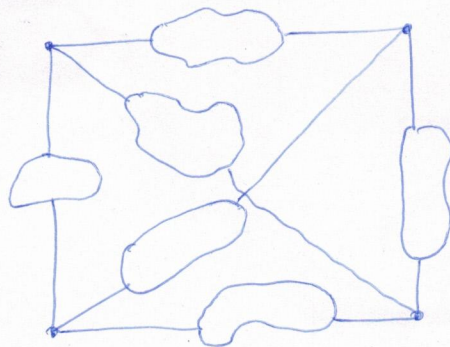


Figure 3

- ④ If the two circuits in Fig. 4 are equivalent as seen from the 2 terminals, find v_{Th} and R_{Th} .

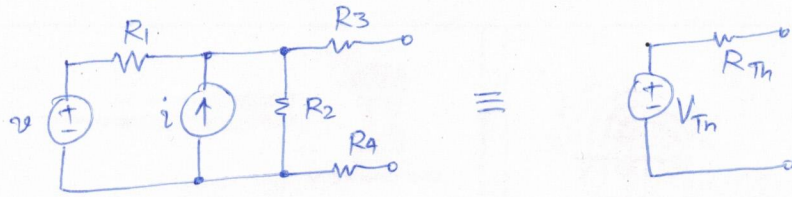


Figure 4

- ⑤ If the two circuits in Fig. 5 are equivalent as seen from the two terminals, find i_{No} and R_{No} .

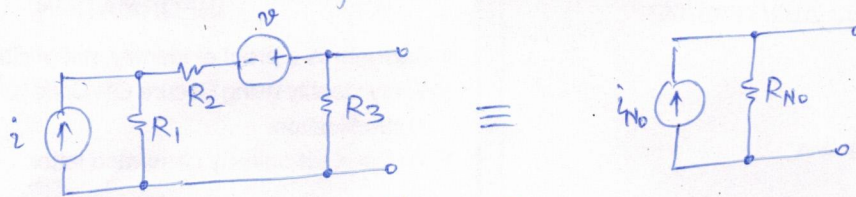


Figure 5

- ⑥ Solve for the voltage across Z_0 in the circuit of Fig. 6.

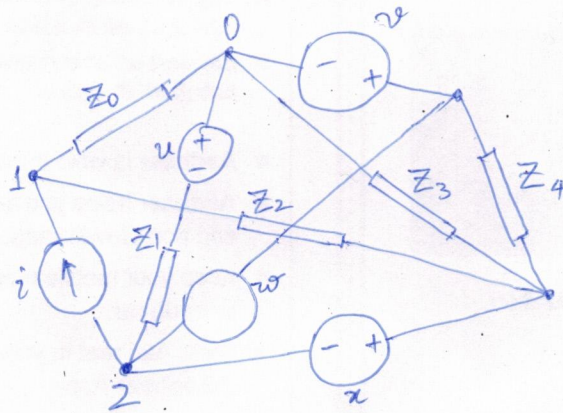


Figure 6

- ⑦ Find voltage at node 0 in the circuit of Fig. 7. Assume $v_1, v_2, v_3,$

$v_4, i_5, R_1, R_2, L_3, C_4, R_6$ are all known.

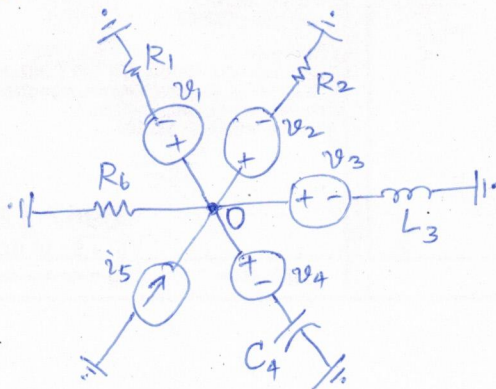


Figure 7

⑧ Find (i) R_L given R_s , and (ii) R_s given R_L , for

(a) maximum power transfer from source v_s to load R_L ;

(b) maximum efficiency.

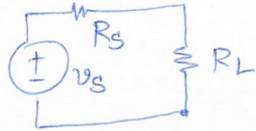


Figure 8